

1. A VSWR of 1 indicates:

- a) A perfectly matched line.
- b) A completely mismatched line.
- c) Maximum power transfer.
- d) Both a and c. **Answer: d)**

2. The input impedance of a transmission line terminated in a load impedance Z_L is:

- a) Z_L
- b) Z_0
- c) $Z_0 [(Z_L + jZ_0 \tan(\beta l)) / (Z_0 + jZ_L \tan(\beta l))]$
- d) $Z_L [(Z_0 + jZ_L \tan(\beta l)) / (Z_L + jZ_0 \tan(\beta l))]$ **Answer: c)**

3. The attenuation constant (α) represents:

- a) The loss of power or voltage along the transmission line.
- b) The phase shift along the transmission line.
- c) The reflection coefficient.
- d) The VSWR. **Answer: a)**

4. If the frequency is doubled, how does the skin depth change?

- a) Doubles
- b) Remains the same
- c) Decreases by a factor of $\sqrt{2}$
- d) Increases by a factor of $\sqrt{2}$ **Answer: c)**

5. If the transmission line length is an integer multiple of half-wavelengths, the input impedance will be:

- a) Equal to the load impedance
- b) Infinite
- c) Zero
- d) Equal to the characteristic impedance

Answer: a)

6. If the VSWR is 2, the reflection coefficient is approximately:

- a) 0.33
- b) 0.5
- c) 0.67
- d) 1

Answer: a)

7. A transmission line has a Z_0 of 75 ohms and a load of 25 ohms. The VSWR is:

- a) 0.333
- b) 3

- c) 2
- d) 1 **Answer: b)**

8. The purpose of impedance matching in a transmission line system is to:

- a) Maximize power transfer to the load.
- b) Minimize reflections.
- c) Improve signal quality.
- d) All of the above. **Answer: d)**

9. A normalized impedance $Z=0.5+j0.5$ is located in which region of the Smith Chart?

- a) Right half-plane
- b) Left half-plane
- c) Upper half-plane
- d) Lower half-plane

Answer: c) Upper half-plane

10. A quarter-wave transformer is used to:

- a) Match impedance between two different transmission lines
- b) Increase the frequency of signals
- c) Act as a band-stop filter
- d) Attenuate signals

Answer: a)

11. The center of the Smith chart represents:

- a) $Z_L = 0$
- b) $Z_L = \infty$
- c) $Z_L = Z_0$
- d) $Z_L = 2Z_0$ **Answer: c)**

12. A transmission line has a characteristic impedance (Z_0) of 50 ohms and is terminated in a load impedance (Z_L) of 100 ohms. The reflection coefficient (Γ) at the load is:

- a) 0.333
- b) 0.5
- c) 1
- d) -0.333 **Answer: a)**

13. A lossless transmission line has a Z_0 of 50 ohms. If the input impedance at a certain point is $100 + j50$ ohms, calculate the normalised impedance located on a smiths chart :

- a) $2 + j1$
- b) $1 + j0.5$
- c) $0.5 + j0.25$
- d) $2 - j1$ **Answer: a)**

14. A transmission line is terminated in a short circuit. What is the VSWR?

- a) 1
- b) Infinity
- c) 2
- d) 0

Answer b

15. A lossless transmission line has $V_{\text{incident}}=10$ V and $V_{\text{reflected}}=2$ V. What is the reflection coefficient?

- a) 0.1
 - b) 0.2
 - c) 0.3
 - d) 0.4
- Answer:** b) 0.2

16. A normalized impedance $Z=1+j0$ is located at which point on the Smith Chart?

- a) The leftmost point
- b) The rightmost point
- c) The center
- d) The topmost point

Answer: c) The center

17. A load has a normalized impedance $Z_L=2+j1$. What is the corresponding normalized admittance Y_L ?

- a) $0.4-j0.2$
 - b) $0.5-j0.5$
 - c) $0.2-j0.4$
 - d) $0.3-j0.3$
- Answer:** a)

18. When moving along a transmission line towards the load, what happens to the reflection coefficient?

- a) Increases
- b) Decreases
- c) Remains the same
- d) Becomes negative

Answer: c) Remains the same

19. What happens to the reflection coefficient when a quarter-wave transformer is used for matching?

- a) It is minimized
- b) It is inverted
- c) It is increased
- d) It is eliminated completely

Answer: b) It is inverted

20. How is the Smiths chart different for Admittance and Impedance calculations:

- a) Shifted clockwise by 90°
 - b) Shifted anti-clockwise by 90°
 - c) Shifted by 180°
 - d) No change
- Answer:** c)